



PARSHVANATH CHARITABLE TRUST'S

A.P. SHAH INSTITUTE OF TECHNOLOGY


Department of Computer Science and Engineering
Data Science

8086 DESIGNING



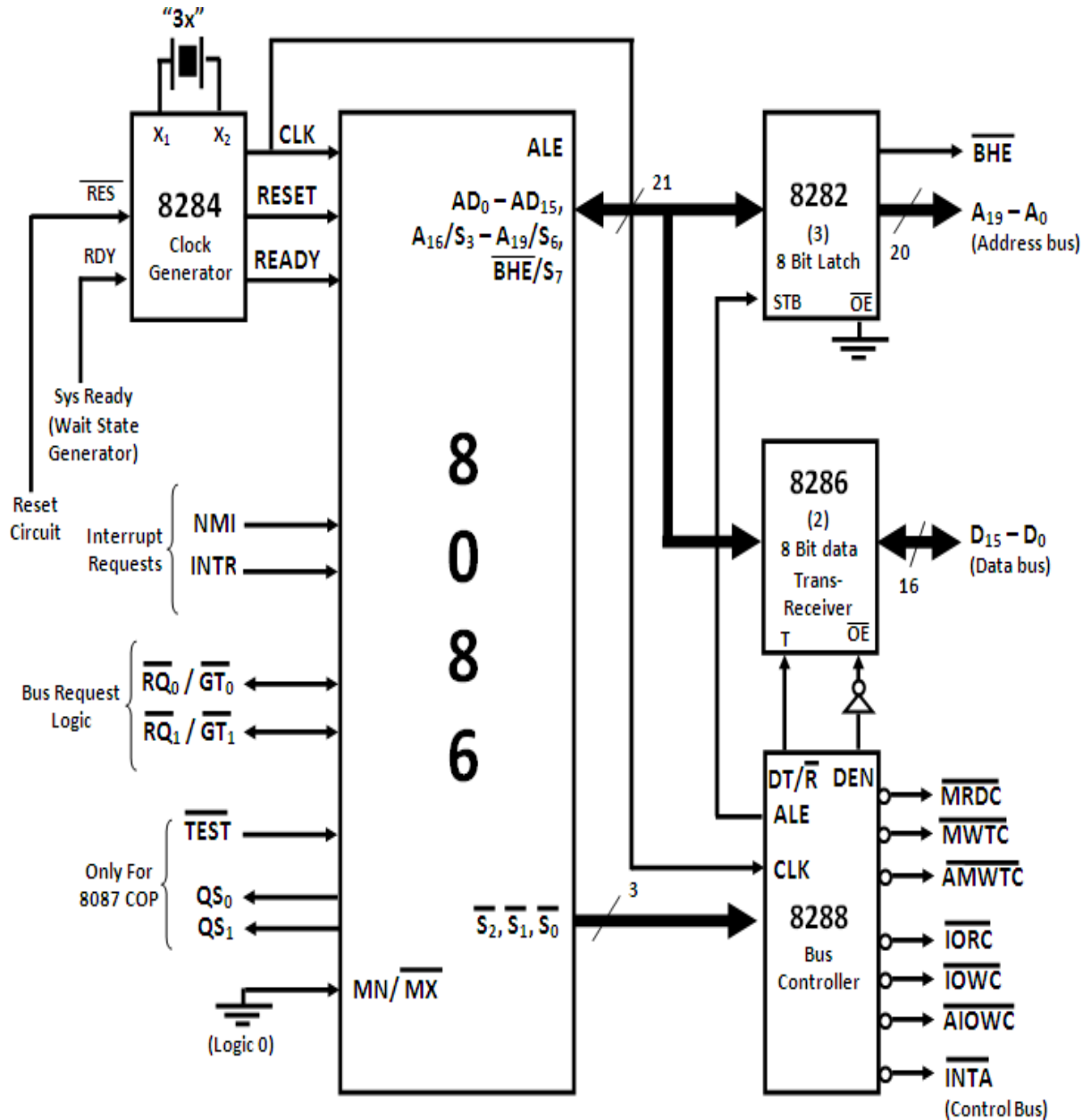**Q1) Design an 8086 based Maximum Mode system working at 6 MHz having the following:
32KB EPROM using 16KB chips,
128KB RAM using 32KB chips,**

Soln: Show 8086 max mode config with a crystal of 18 MHZ.



**Memory Calculations:****EPROM:**

Required = 32 KB, Available = 16 KB

No. of chips = 2 chips.

Starting address of EPROM is calculated as:

FFFFFH – (Space required by total EPROM of 32 KB)

$$\begin{array}{r} \text{F F F F F H} \\ - \text{7 F F F H} \\ \hline \text{F 8 0 0 0 H} \end{array}$$

Size of a single EPROM chip = 16 KB

$$\begin{aligned} &= 16 \times 1\text{KB} = 2^4 \times 2^{10} \\ &= 2^{14} \\ &= \underline{14} \text{ address lines} \\ &= \underline{\text{(A14 ... A1)}} \end{aligned}$$

RAM:

Required = 128 KB, Available = 32 KB

No. of chips = 4 chips.

Starting address of RAM is: 00000H

$$\begin{aligned} \text{Size of a single RAM chip} &= 32 \text{ KB} \\ &= 32 \times 1 \text{ KB} = 2^5 \times 2^{10} \\ &= 2^{15} \\ &= \underline{15} \text{ address lines} \\ &= \underline{\text{(A15 ... A1)}} \end{aligned}$$

[illegible]




PARSHVANATH CHARITABLE TRUST'S

A.P. SHAH INSTITUTE OF TECHNOLOGY

Department of Computer Science and Engineering

Data Science

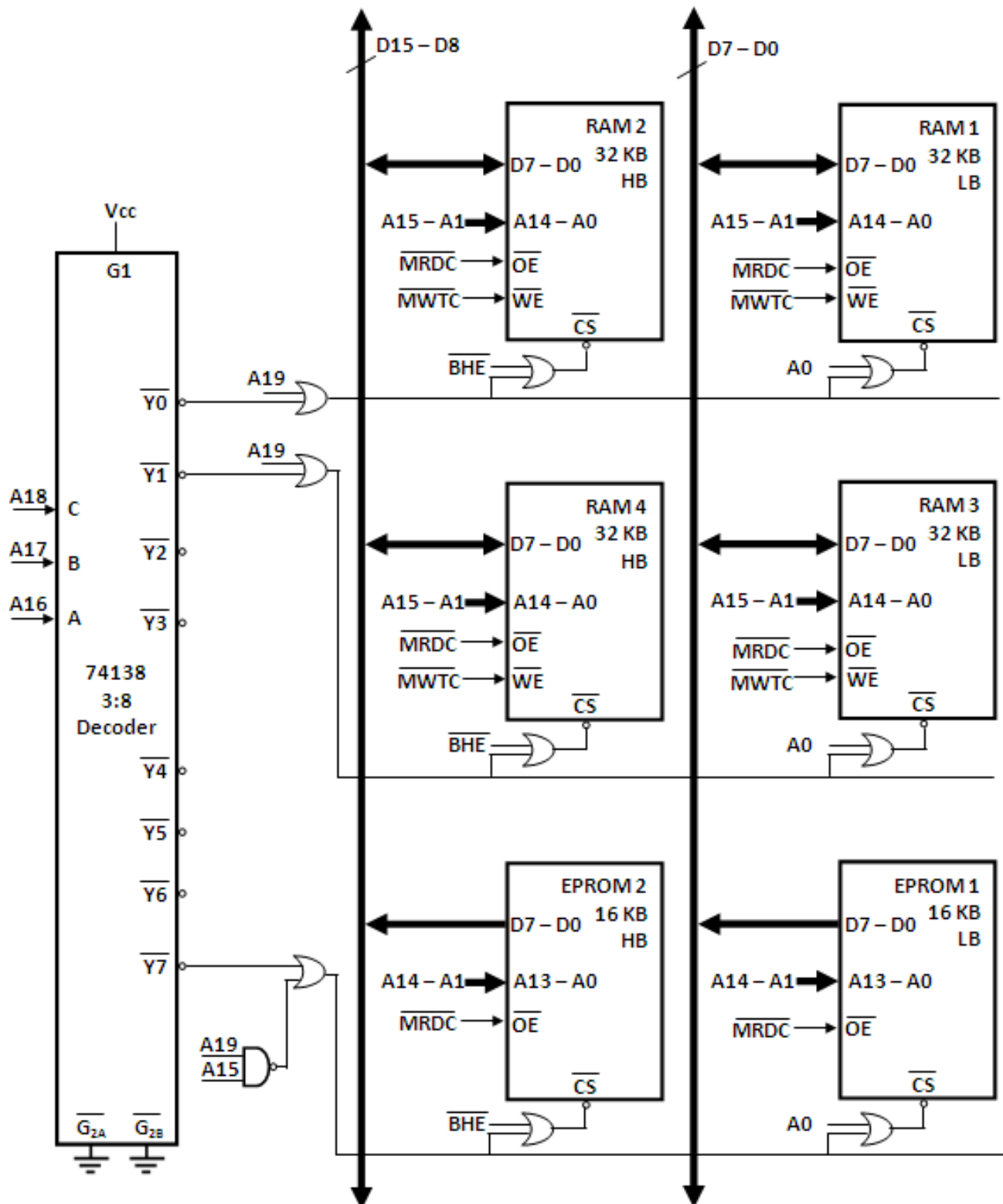



PARSHVANATH CHARITABLE TRUST'S

A.P. SHAH INSTITUTE OF TECHNOLOGY

Department of Computer Science and Engineering
Data Science



PARSHVANATH CHARITABLE TRUST'S

A.P. SHAH INSTITUTE OF TECHNOLOGY

Department of Computer Science and Engineering
Data Science
